


Digital Logic & Design

Dr. Waseem Ikram

Lecture 06




NOR Universal Gate

Input		Output
A	B	F
0	0	0
0	1	1
1	0	1
1	1	1




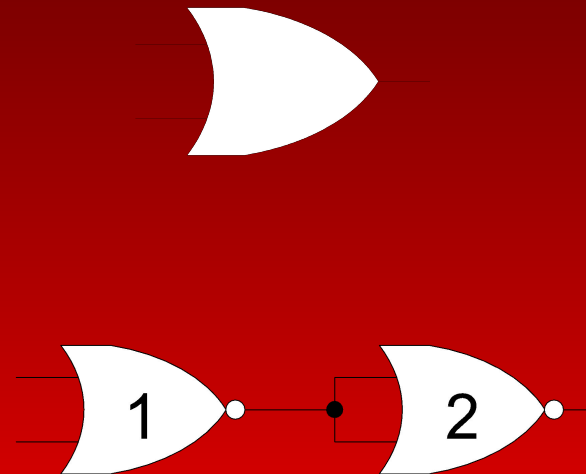


NOR Universal Gate

Input		Output
A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

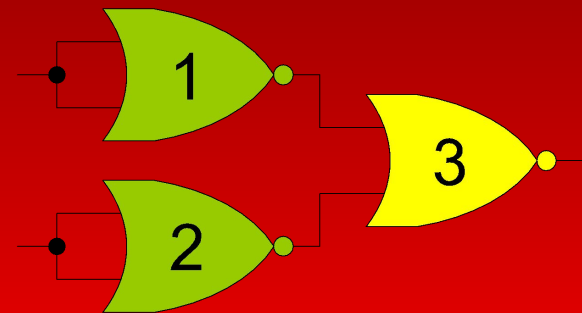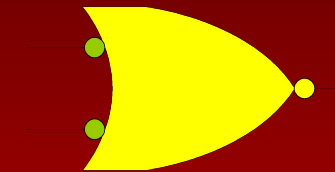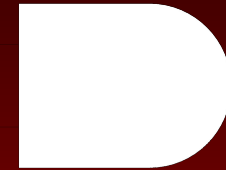


NAND-NOR Universal Gate

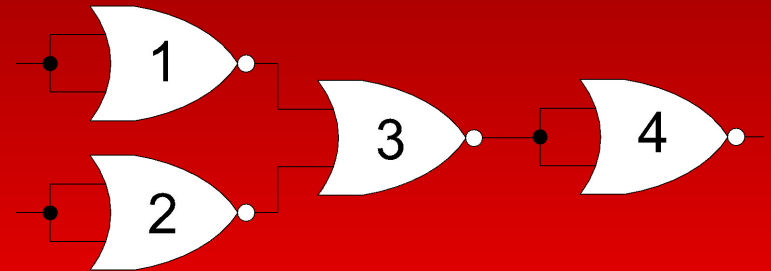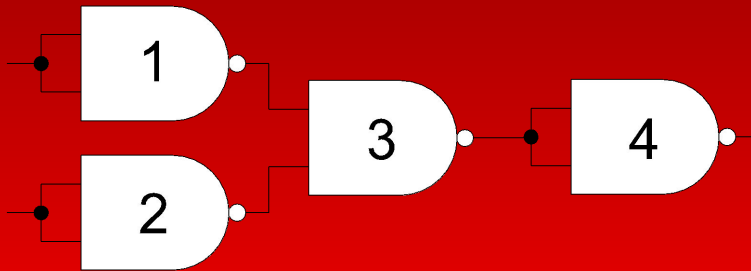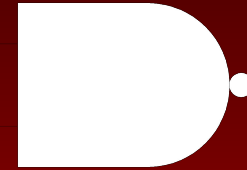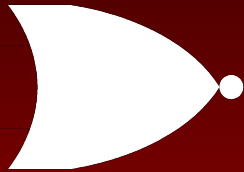

XOR Gate

- 1 output
- 2 inputs
- Multiple inputs

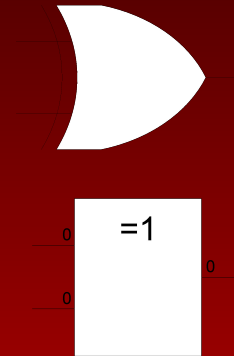


XOR Gate function

Input		Output
A	B	F
0	0	0
0	1	1
1	0	1
1	1	0



$$F = A \oplus B$$

XOR Gate Timing Diagram

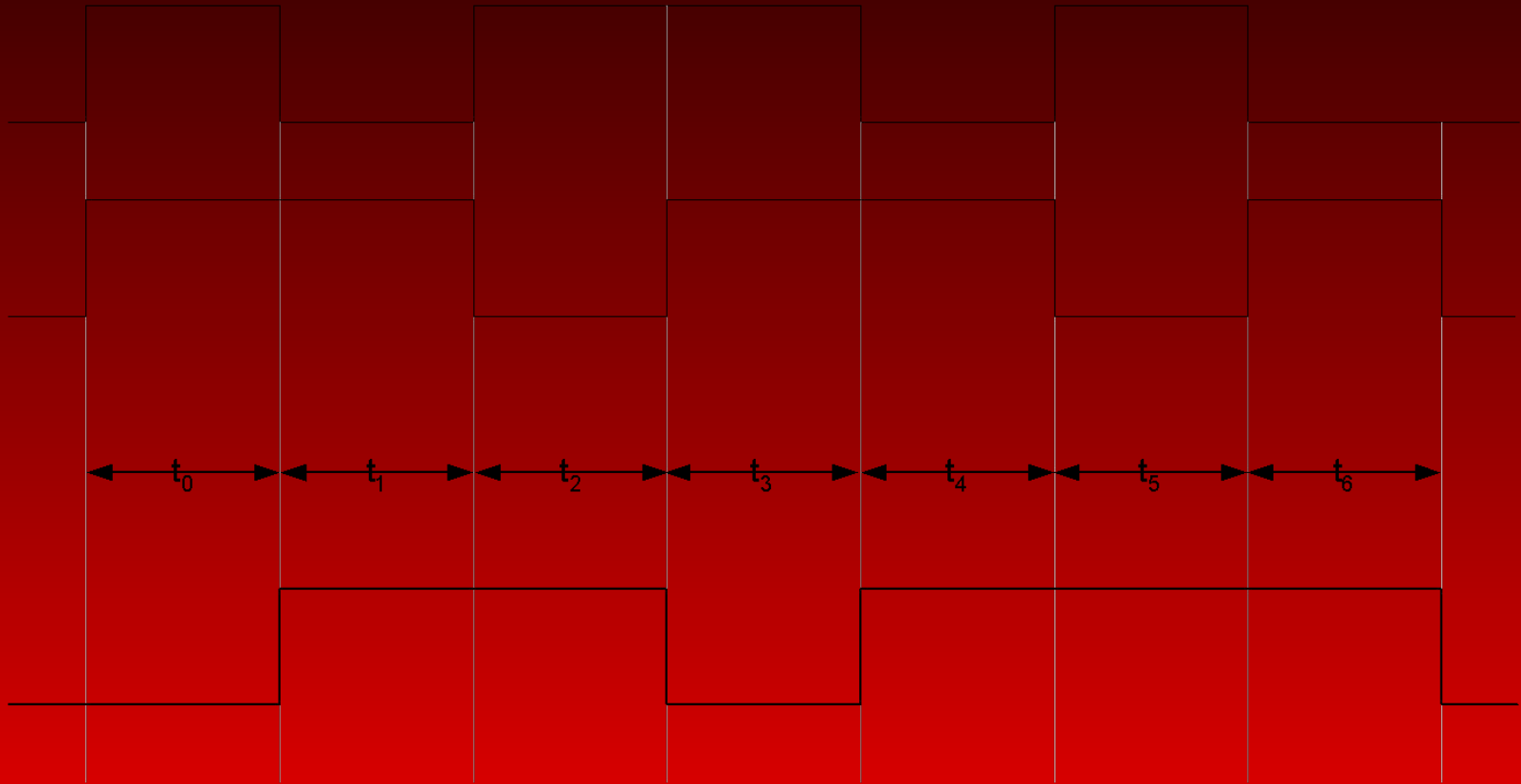

XNOR Gate

- 1 output
- 2 inputs
- Multiple inputs

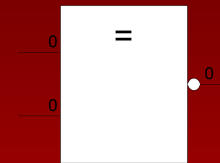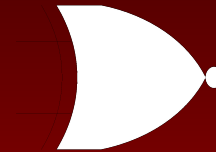


XNOR Gate function


Input		Output
A	B	F
0	0	1
0	1	0
1	0	0
1	1	1

$$F = \overline{A \oplus B}$$


XNOR Gate Timing Diagram

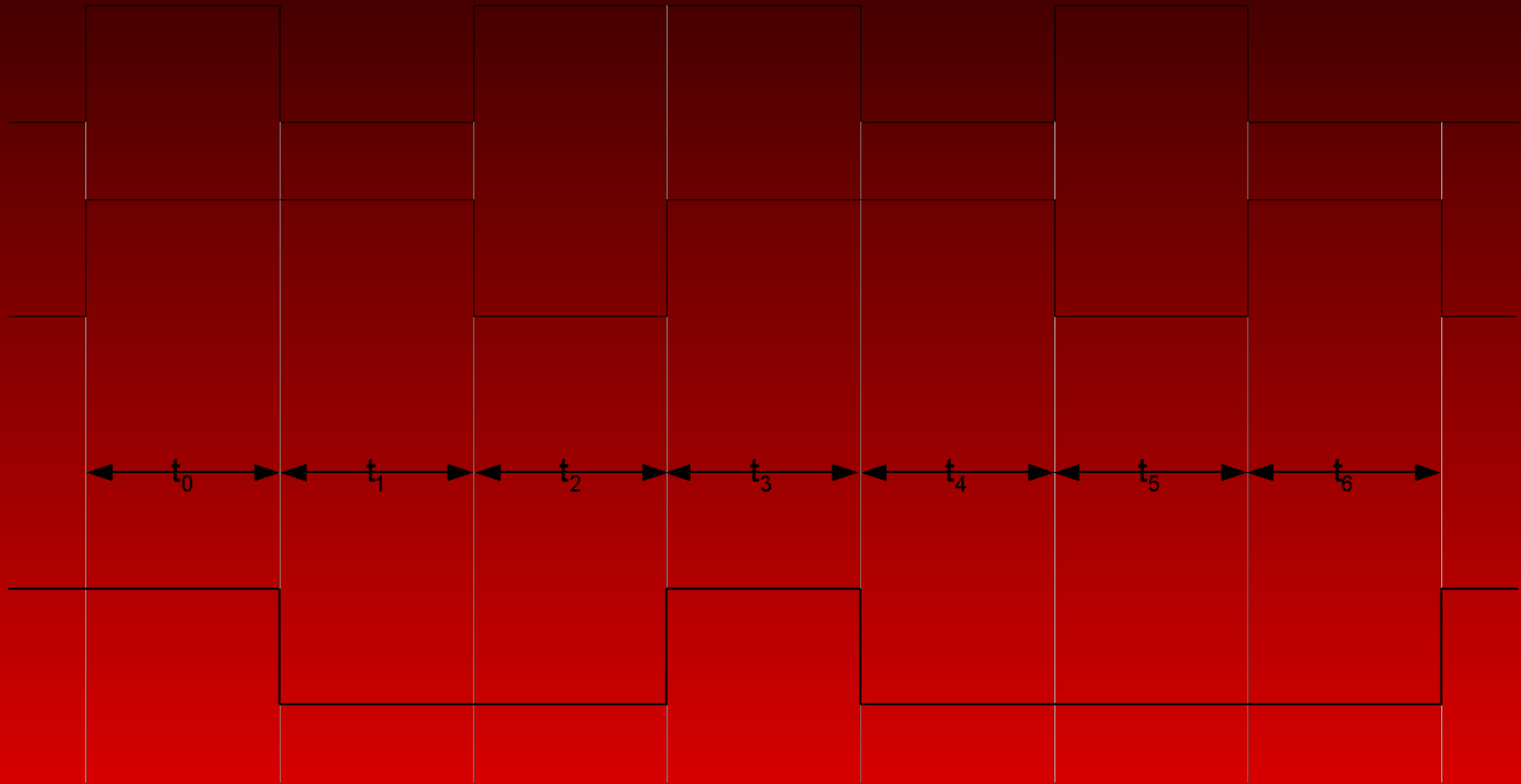


Logic Gate Integrated Circuits

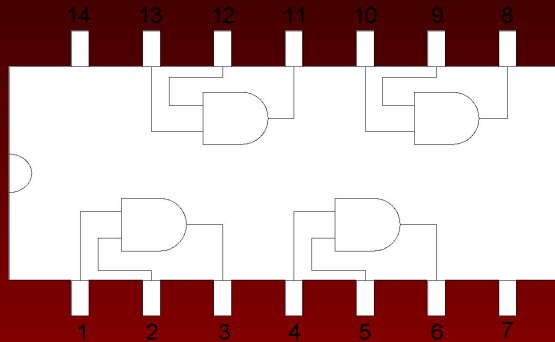


7408
Four 2-Input AND Gate

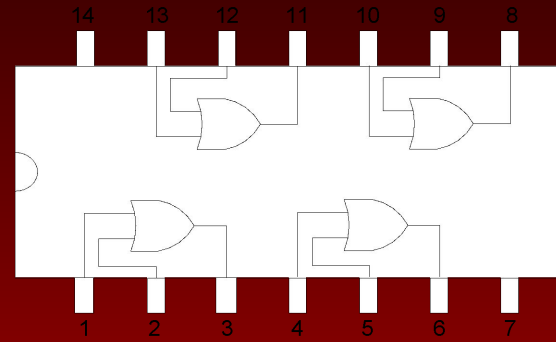

7432
Four 2-Input OR Gate

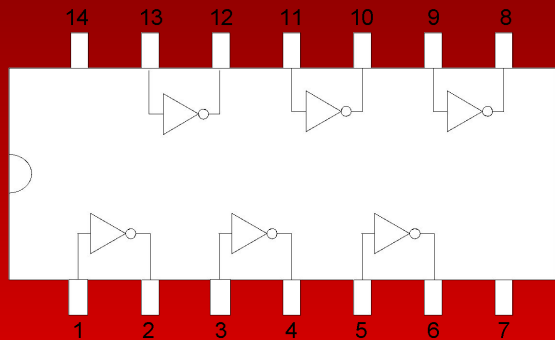


7404
Hex Inverters

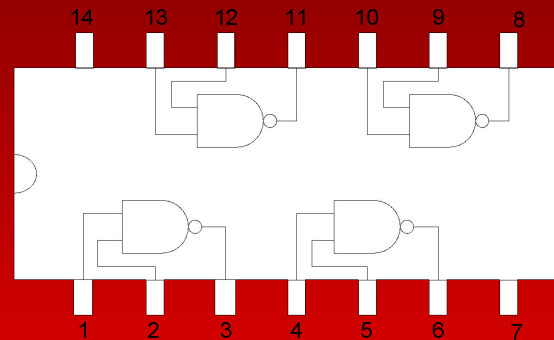


7400
Four 2-Input NAND Gate


Logic Gate Integrated Circuits

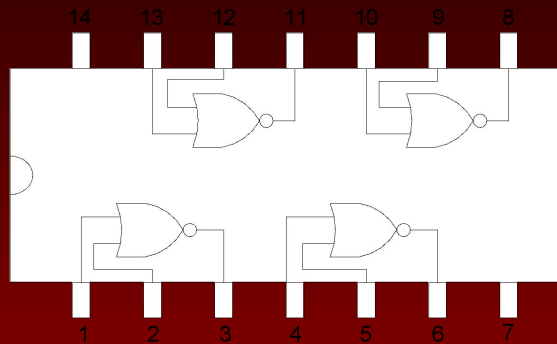

7402
Four 2-Input NOR Gate

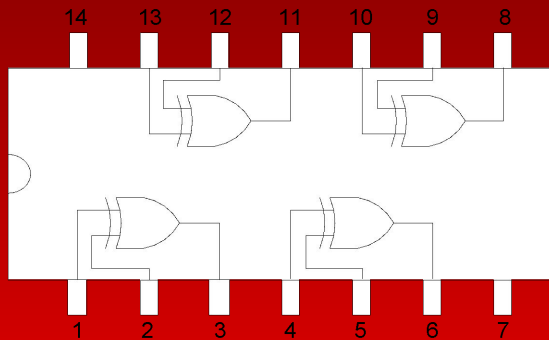

7486
Four 2-Input XOR Gate

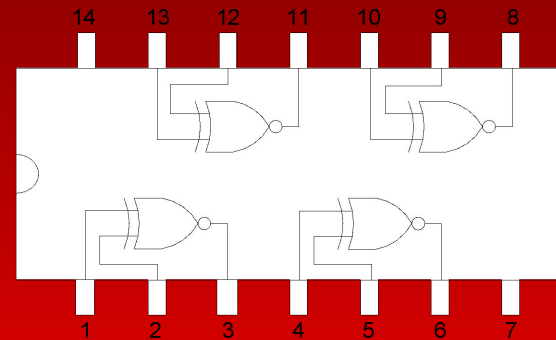

74266
Four 2-Input XNOR Gate