

Digital circuits



Combinational circuit

Output depends only on present inputs

Half and Full Adders

Comparator

Decoder

Encoder

Code Converter

Multiplexer(Data
Selector)

De multiplexers

Sequential circuit

**Output depends upon present inputs as well as
previous output**

Latches



Flip-Flops

The Half-Adder

0	+	0	=	0
0	+	1	=	1
1	+	0	=	1
1	+	1	=	10

A half-adder adds two bits and produces a sum and an output carry.

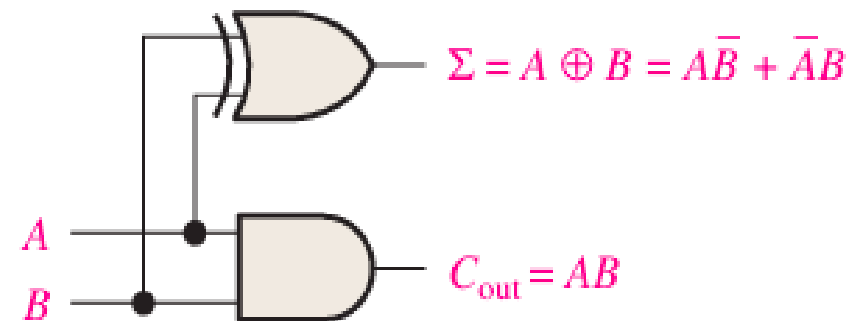
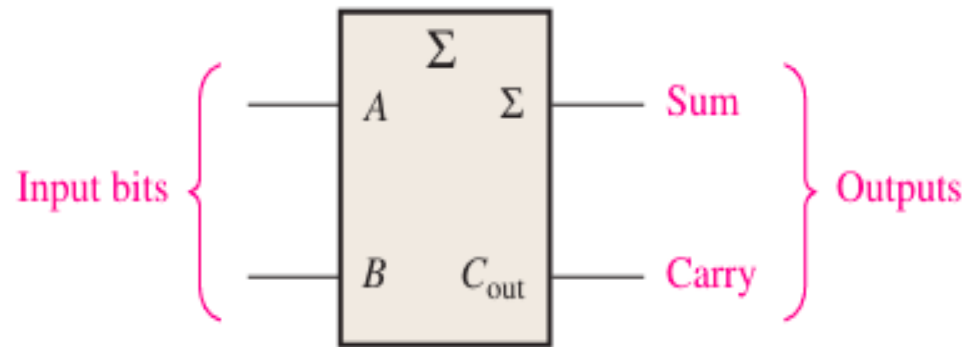
The half-adder accepts two binary digits on its inputs and produces two binary digits on its outputs—a sum bit and a carry bit.



Half Adder

Digital computers and calculators consist of arithmetic and logic circuits. The basic building blocks of the arithmetic unit in a digital computer are adders.

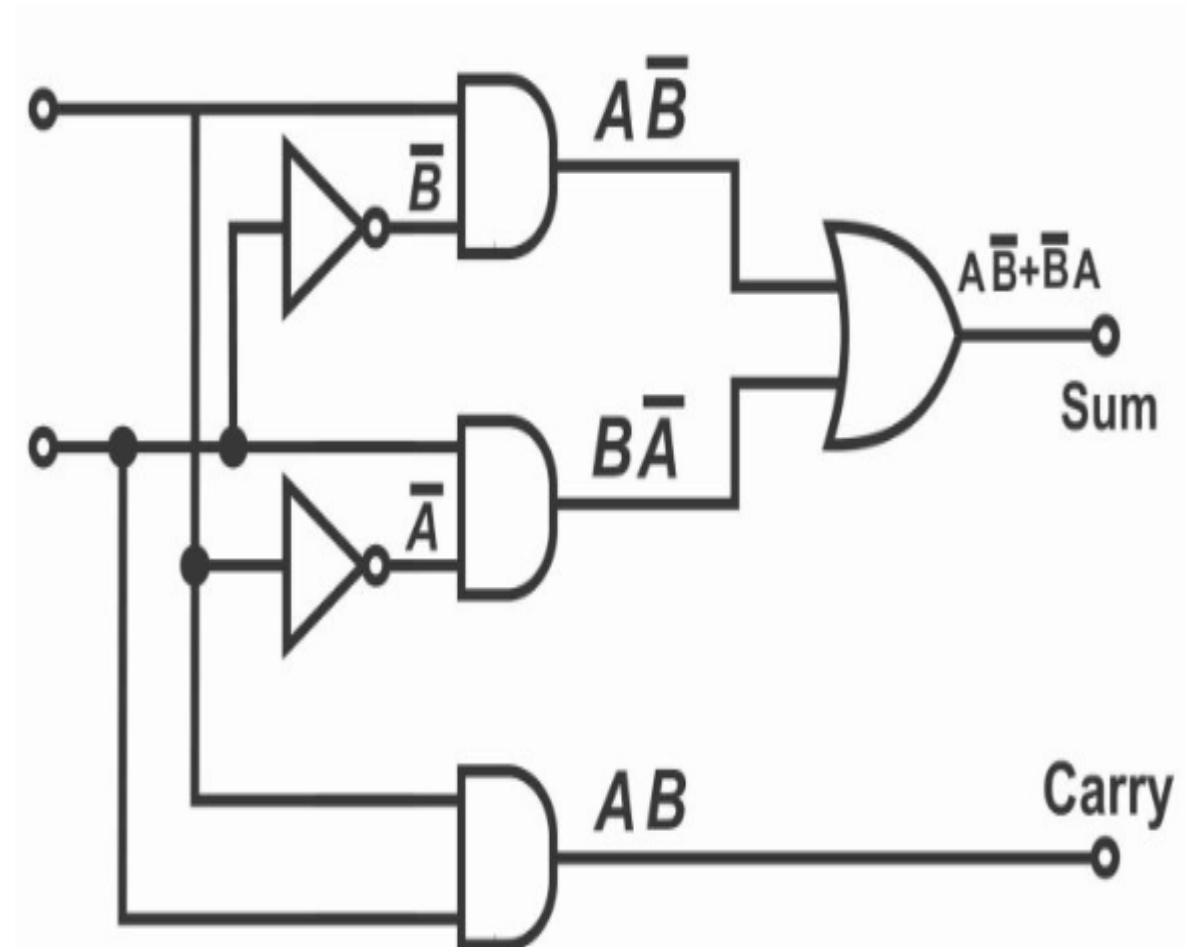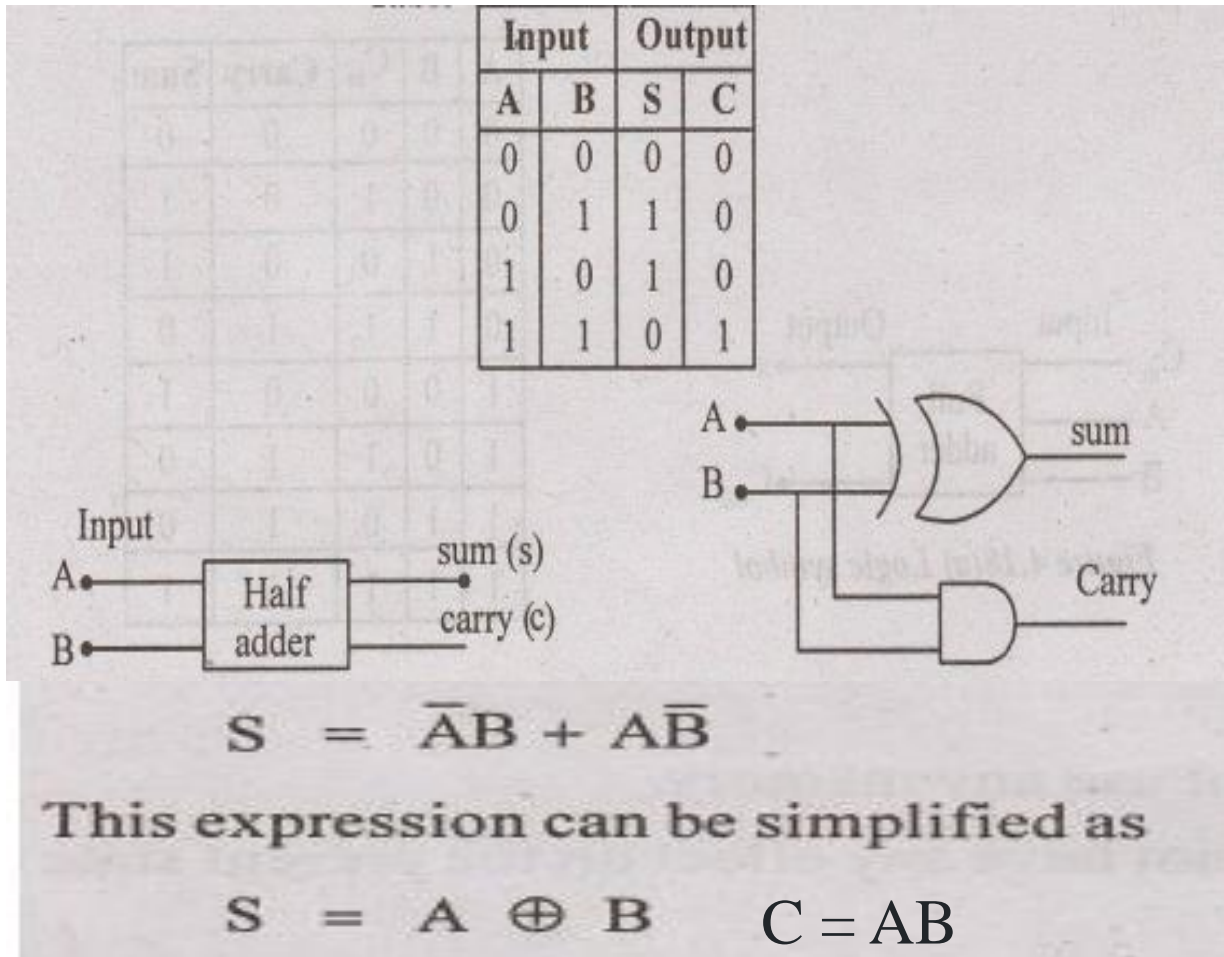The simplest combinational circuit that performs the arithmetic addition of two binary digits is called a half-adder. A half adder has two inputs and two outputs.




Full Adder

A half-adder has only two inputs, and there is no provision to add a carry coming from the lower-order bits when multi-bit addition is performed. For this purpose, a full-adder is designed.


A full adder is a combinational circuit that performs the arithmetic sum of three input bits and produces a sum output and a carry.

$$\Sigma = (A \oplus B) \oplus C_{in}$$


$$C_{out} = AB + (A \oplus B)C_{in}$$

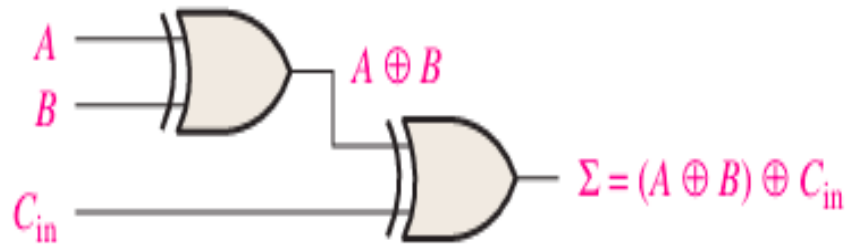

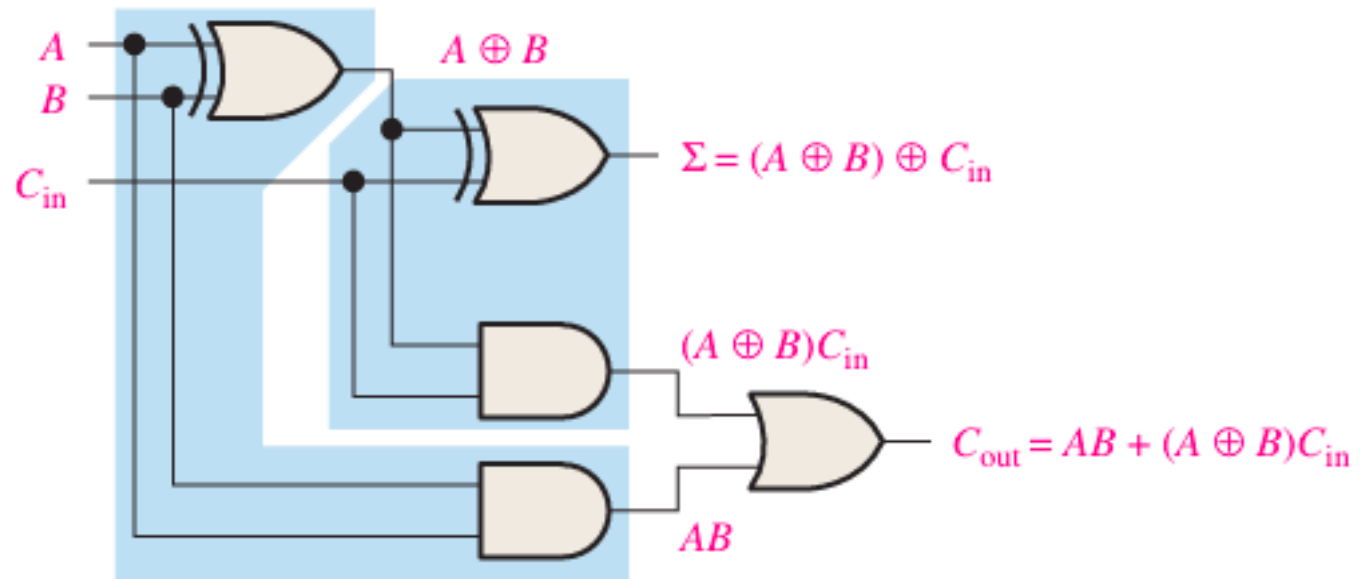
(a) Logic required to form the sum of three bits



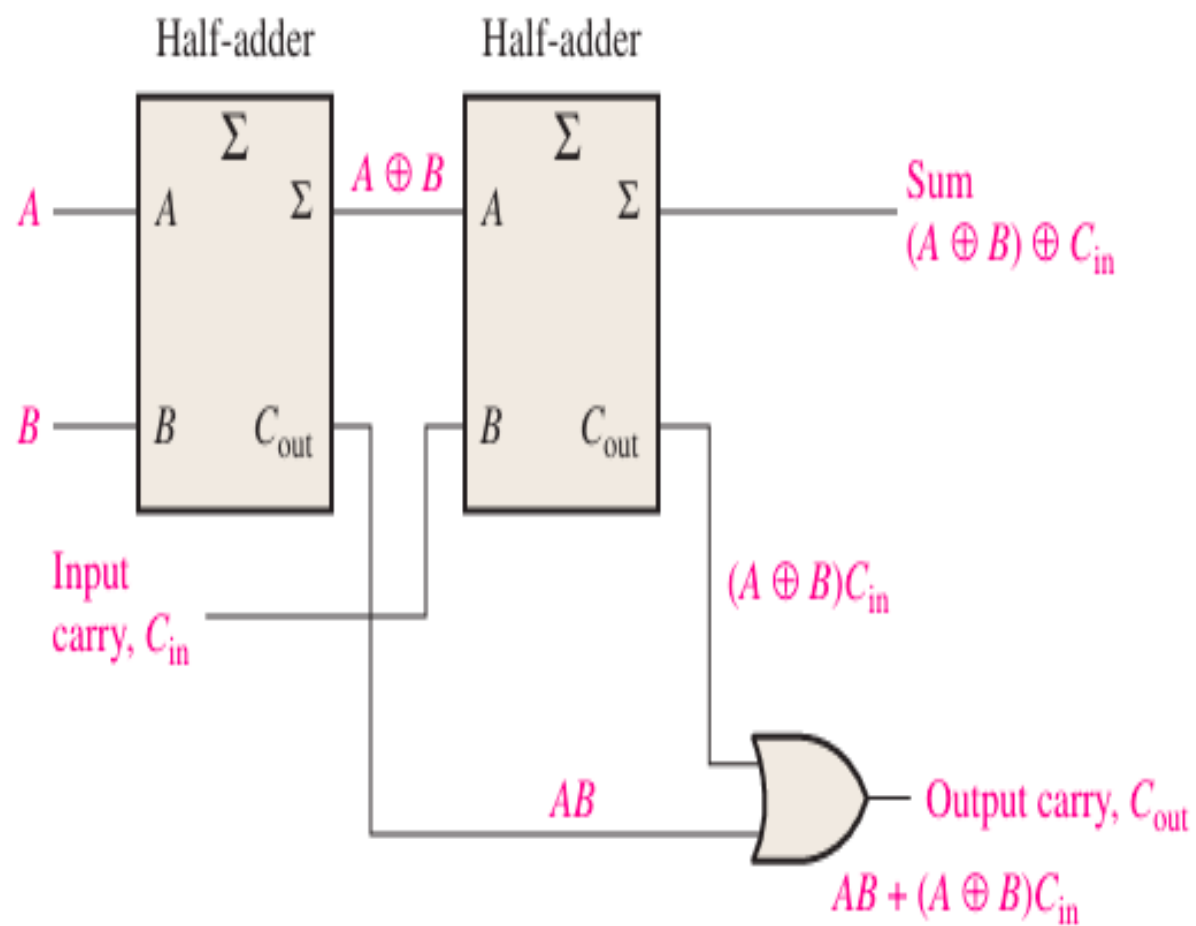(b) Complete logic circuit for a full-adder (each half-adder is enclosed by a shaded area)




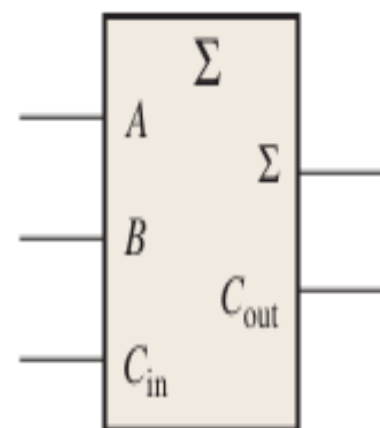(a) Arrangement of two half-adders to form a full-adder




(b) Full-adder logic symbol


A	B	C_{in}	Carry	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

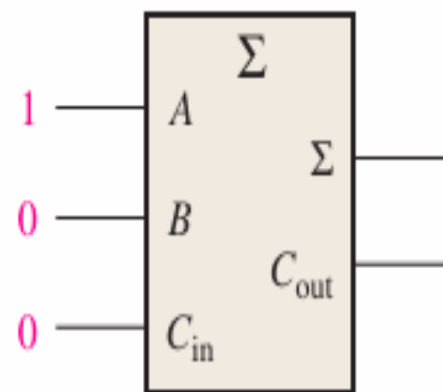

(a)

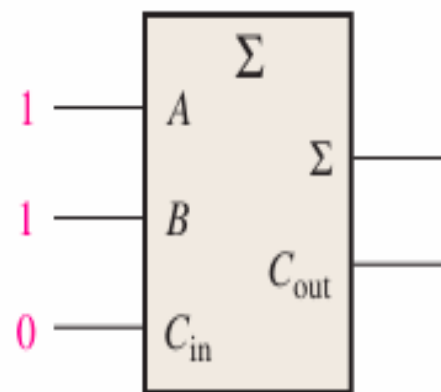

(b)

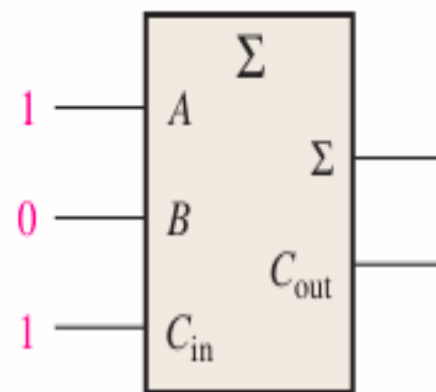

(c)

Solution

(a) The input bits are $A = 1$, $B = 0$, and $C_{in} = 0$.

$$1 + 0 + 0 = 1 \text{ with no carry}$$

Therefore, $\Sigma = \mathbf{1}$ and $C_{out} = \mathbf{0}$.

(b) The input bits are $A = 1$, $B = 1$, and $C_{in} = 0$.

$$1 + 1 + 0 = 0 \text{ with a carry of } 1$$

Therefore, $\Sigma = \mathbf{0}$ and $C_{out} = \mathbf{1}$.

(c) The input bits are $A = 1$, $B = 0$, and $C_{in} = 1$.

$$1 + 0 + 1 = 0 \text{ with a carry of } 1$$

Therefore, $\Sigma = \mathbf{0}$ and $C_{out} = \mathbf{1}$.

Parallel Binary Adders

Two or more full-adders are connected to form parallel binary adders.


Carry bit from right column

$$\begin{array}{r} 1 \\ 11 \\ + 01 \\ \hline 100 \end{array}$$

In this case, the carry bit from second column becomes a sum bit.

General format, addition of two 2-bit numbers:
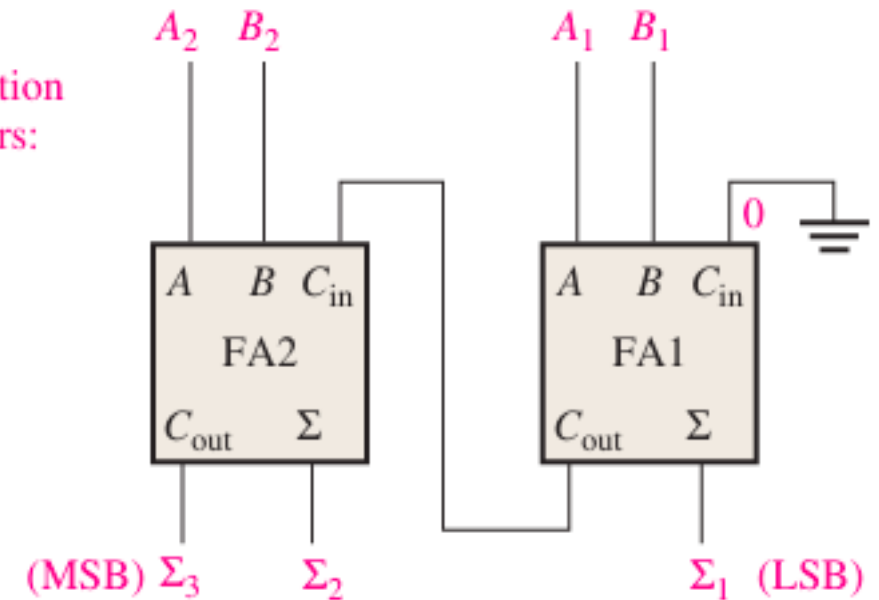
$$\begin{array}{r} A_2A_1 \\ + B_2B_1 \\ \hline \Sigma_3\Sigma_2\Sigma_1 \end{array}$$




Four-Bit Parallel Adders

A group of four bits is called a nibble.


A basic 4-bit parallel adder is implemented with four full-adder.

Again, the LSBs (A1 and B1) in each number being added go into the right-most full-adder; the higher-order bits are applied to the successively higher-order adders, with the MSBs (A4 and B4) in each number being applied to the left-most full-adder.

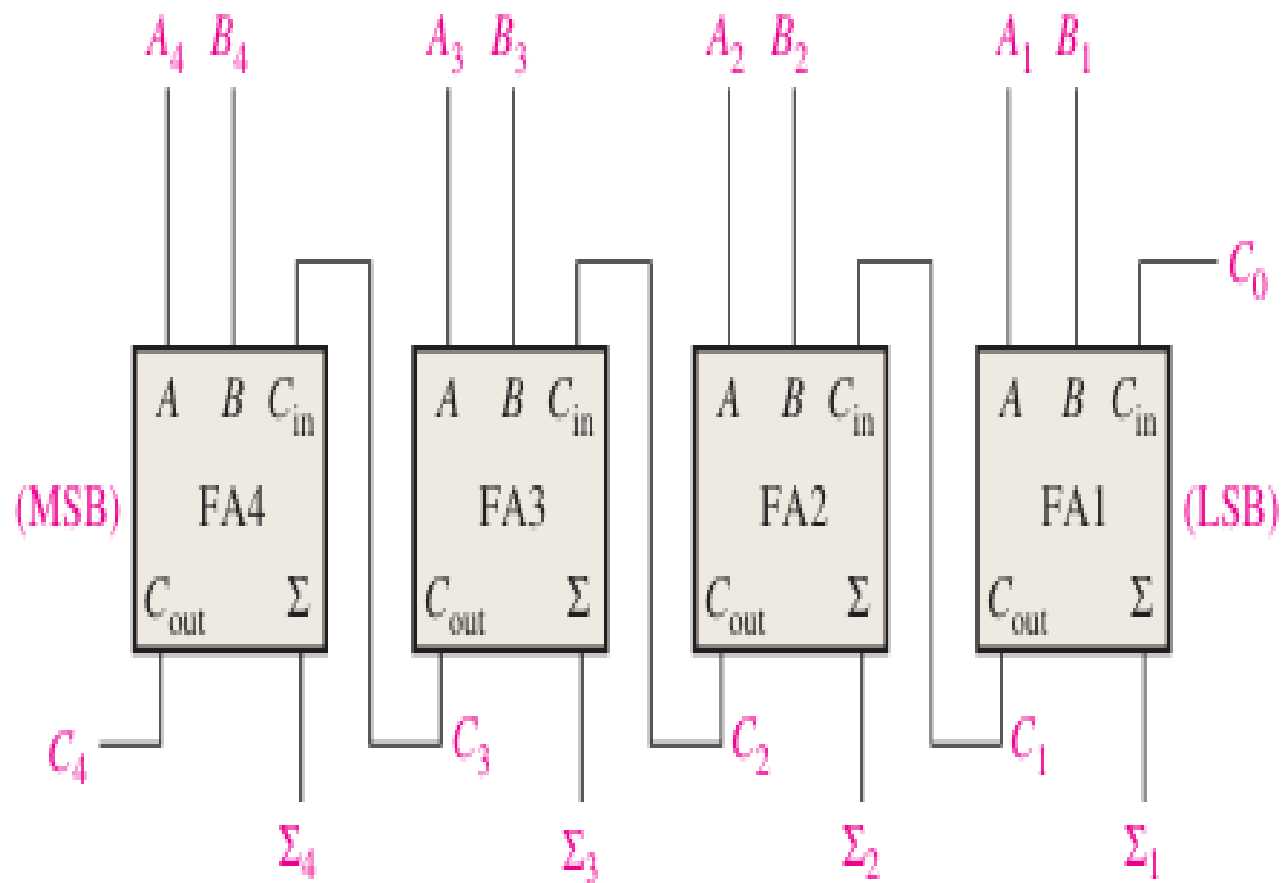The carry output of each adder is connected to the carry input of the next higher-order adder. These are called internal carries.



(a) Block diagram

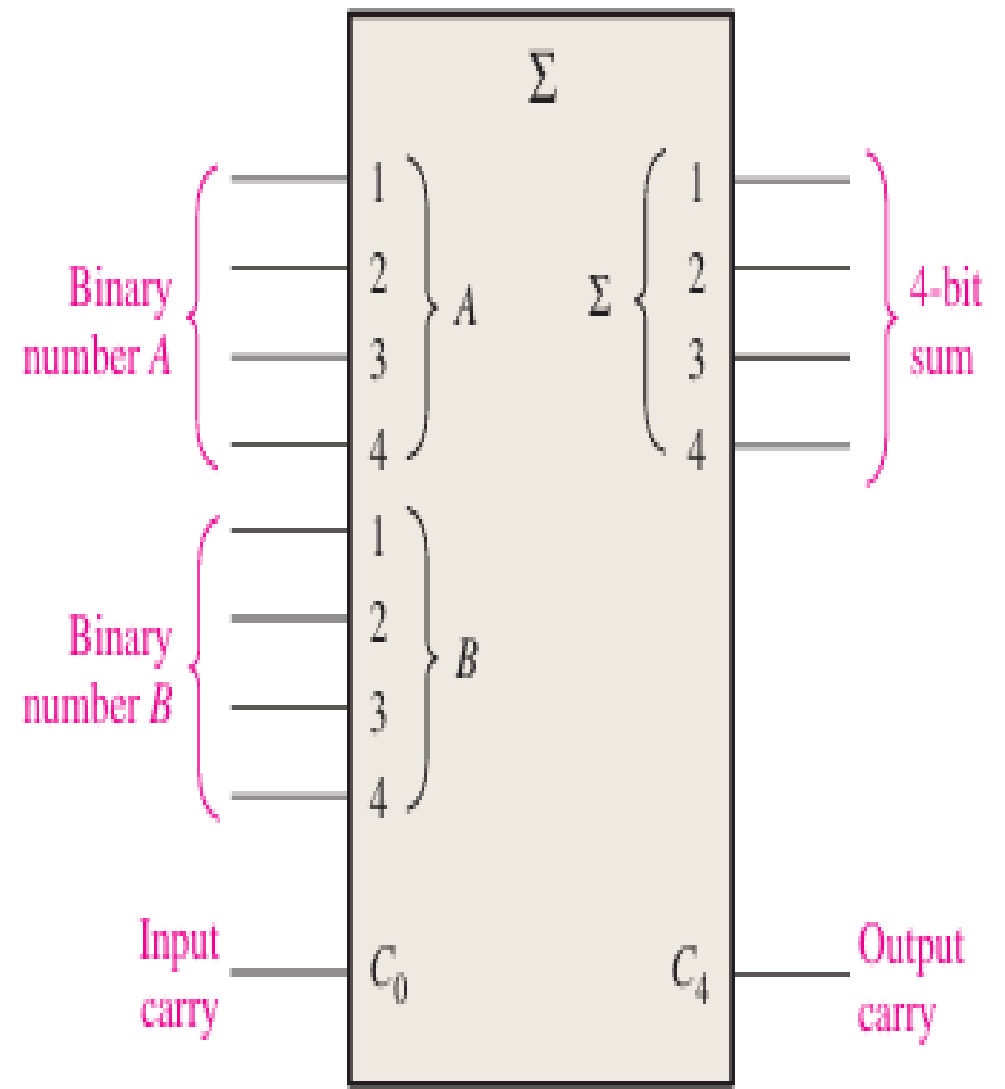

(b) Logic symbol

Truth Table for a 4-Bit Parallel Adder

Truth table for each stage of a 4-bit parallel adder.

C_{n-1}	A_n	B_n	Σ_n	C_n
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Use the 4-bit parallel adder truth table to find the sum and output carry for the addition of the following two 4-bit numbers if the input carry (C_{n-1}) is 0:

$$A_4A_3A_2A_1 = 1100 \quad \text{and} \quad B_4B_3B_2B_1 = 1100$$

Solution

For $n = 1$: $A_1 = 0$, $B_1 = 0$, and $C_{n-1} = 0$. From the 1st row of the table,

$$\Sigma_1 = 0 \quad \text{and} \quad C_1 = 0$$

For $n = 2$: $A_2 = 0$, $B_2 = 0$, and $C_{n-1} = 0$. From the 1st row of the table,

$$\Sigma_2 = 0 \quad \text{and} \quad C_2 = 0$$

For $n = 3$: $A_3 = 1$, $B_3 = 1$, and $C_{n-1} = 0$. From the 4th row of the table,

$$\Sigma_3 = 0 \quad \text{and} \quad C_3 = 1$$

For $n = 4$: $A_4 = 1$, $B_4 = 1$, and $C_{n-1} = 1$. From the last row of the table,

$$\Sigma_4 = 1 \quad \text{and} \quad C_4 = 1$$


C_4 becomes the output carry; the sum of 1100 and 1100 is 11000.

Adder Expansion

Adders can be expanded to handle more bits by cascading.

The 4-bit parallel adder can be expanded to handle the addition of two 8-bit numbers by using two 4-bit adders.

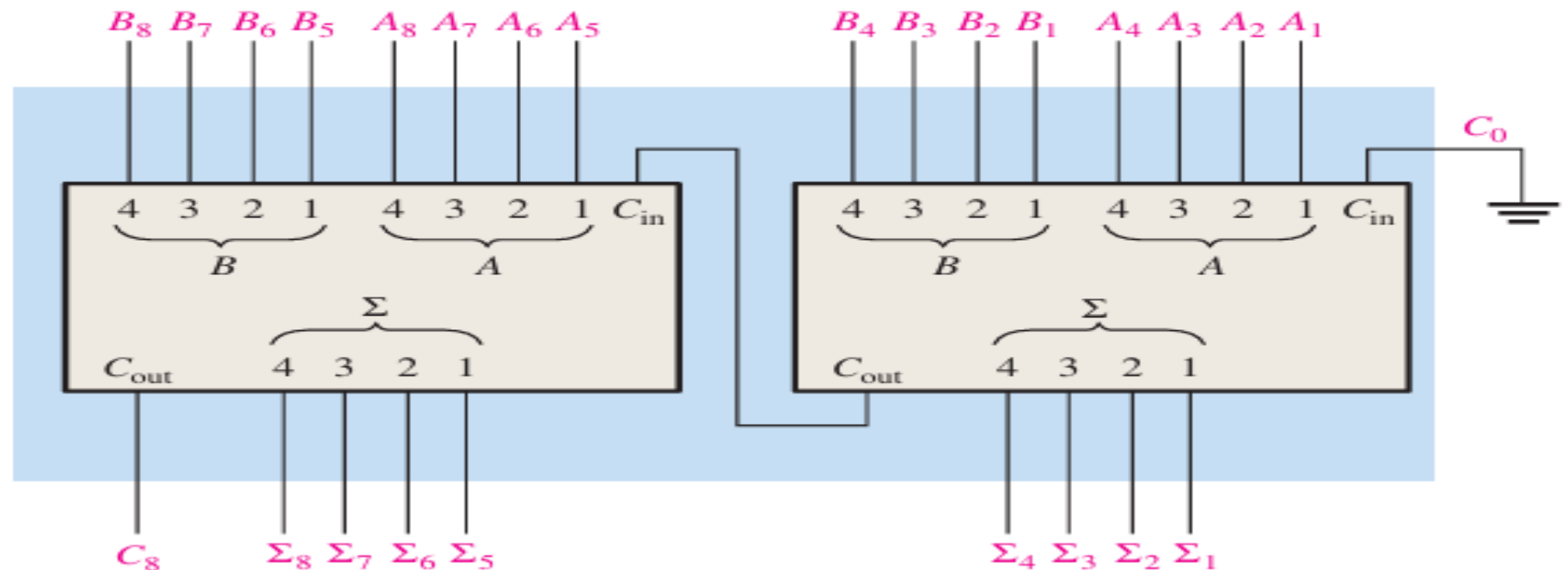The carry input of the low-order adder (C_0) is connected to ground because there is no carry into the least significant bit position, and the carry output of the low-order adder is connected to the carry input of the high-order adder. This process is known as cascading. Notice that, in this case, the output carry is designated C_8 because it is generated from the eighth bit position.



Ripple Carry and Look-Ahead Carry Adders

The Ripple Carry Adder

- A ripple carry adder is one in which the carry output of each full-adder is connected to the carry input of the next higher-order stage (a stage is one full-adder).
- The sum and the output carry of any stage cannot be produced until the input carry occurs; this causes a time delay in the addition process.
- The carry propagation delay for each full-adder is the time from the application of the input carry until the output carry occurs, assuming that the A and B inputs are already present.

