

# Digital Logic & Design

Mr. Abdul Ghafoor

Lecture 05

# Recap


- Number System
- Alternate Representations
  - BCD Code
  - Gray Code
- Alphanumeric Code (ASCII)
- Error Detection using Parity Bit

# Logic Gates

- Basic Building Blocks
- Logic Gate Symbol
- Unique function
- Truth or Function Table
- Function Expression
- Timing Diagram
 
# AND Gate

- 1 output
- 2 inputs
- 3 inputs
- 4 inputs
- Multiple inputs



# AND Gate function


- Logical Multiplication function

| Input |   | Output |
|-------|---|--------|
| A     | B | F      |
| 0     | 0 | 0      |
| 0     | 1 | 0      |
| 1     | 0 | 0      |
| 1     | 1 | 1      |

$$F = A \bullet$$



$$F = A \bullet B \bullet C \bullet \dots$$

# AND Gate Timing Diagram

 
  
# OR Gate

- 1 output
- 2 inputs
- 3 inputs
- 4 inputs
- Multiple inputs



# OR Gate function

- Boolean Add function


| Input |   | Output |
|-------|---|--------|
| A     | B | F      |
| 0     | 0 | 0      |
| 0     | 1 | 1      |
| 1     | 0 | 1      |
| 1     | 1 | 1      |

$$F = A +$$

$$F = A + B + C + ..$$




# OR Gate Timing Diagram

 

# NOT Gate

- 1 input
- 1 output

 


# NOT Gate function

- Invert function

| Input | Output |
|-------|--------|
| A     | F      |
| 0     | 1      |
| 1     | 0      |


$$F = \bar{A}$$

# NOT Gate Timing Diagram

 

 
# AND Gate Applications

- Enable/Disable Device
  - Counter counts when it receives pulses




# OR Gate Applications

- Car door open alarm

 



# NOT Gate Applications

- 1's Complement

 
  
# NAND Gate

- 1 output
- 2 inputs
- 3 inputs
- 4 inputs
- Multiple inputs






# NAND Gate function

- NOT-AND function

| Input |   | Output |
|-------|---|--------|
| A     | B | F      |
| 0     | 0 | 1      |
| 0     | 1 | 1      |
| 1     | 0 | 1      |
| 1     | 1 | 0      |


$$F = \overline{A \bullet B \bullet C}$$

# NAND Gate Timing Diagram

 


# NAND Universal Gate

| Input |   | Output |
|-------|---|--------|
| A     | B | F      |
| 0     | 0 | 1      |
| 0     | 1 | 1      |
| 1     | 0 | 1      |
| 1     | 1 | 0      |

 




# NAND Universal Gate

| Input |   | Output | Output |
|-------|---|--------|--------|
| A     | B | F1     | F      |
| 0     | 0 | 1      | 0      |
| 0     | 1 | 1      | 0      |
| 1     | 0 | 1      | 0      |
| 1     | 1 | 0      | 1      |

 




# NAND Universal Gate

| Input |   | Output |
|-------|---|--------|
| A     | B | F      |
| 0     | 0 | 0      |
| 0     | 1 | 1      |
| 1     | 0 | 1      |
| 1     | 1 | 1      |

   
   
# NOR Gate

- 1 output
- 2 inputs
- 3 inputs
- 4 inputs
- Multiple inputs



# NOR Gate function

- NOT-OR function

| Input |   | Output |
|-------|---|--------|
| A     | B | F      |
| 0     | 0 | 1      |
| 0     | 1 | 0      |
| 1     | 0 | 0      |
| 1     | 1 | 0      |

$$F = \overline{A + B}$$

$$F = \overline{A + B + C + \dots}$$

# NOR Gate Timing Diagram

